

Code Issues Pull requests Actions Projects Wiki Security Insights Settings



Digital-electronics-2 / 07-UART.md



Lab 7: MARIO GOLBANO CORZO

Link to this file in my GitHub repository:

https://github.com/mariogolbi/Digital-electronics-2

Analog-to-Digital Conversion


1. Complete table with voltage divider, calculated, and measured ADC values for all five push buttons.

Push button	PC0[A0] voltage	ADC value (calculated)	ADC value (measured)
Right	0 V	0	0
Up	0.495 V	101	99
Down	1.203 V	246	257
Left	1.970 V	403	410
Select	3.182 V	651	640
none	5 V	1023	1023


2. Code listing of ACD interrupt service routine for sending data to the LCD/UART and identification of the pressed button. Always use syntax highlighting and meaningful comments:

```
* Function: ADC complete interrupt
 * Purpose: Display value on LCD and send it to UART.
 ISR(ADC_vect)
{
   // WRITE YOUR CODE HERE
       uint16_t value=0;
       char lcd_string[4]="0000";
       //Copy ADC result to 16-bit variable
       value = ADC;
       // Clear previous value
       lcd_gotoxy(8,0);
       lcd_puts(" ");
       //Put new value to LCD
       itoa(value,lcd_string,10); //convert decimal value to string
       lcd_gotoxy(8,0);
       lcd_puts(lcd_string);
       // Send the same value to UART
       uart_puts(lcd_string);
       uart_puts(" ");
       // Display value in hexa
       itoa(value,lcd_string,16);
       lcd_gotoxy(13,0);
       lcd_puts(lcd_string);
       // Display what push button was pressed
       itoa(ADC0D,lcd_string,10);
       lcd_gotoxy(8,1);
       lcd_puts(lcd_string);
       uart_puts(lcd_string);
       uart putc('\n');
       uart_putc('\r');
}
```

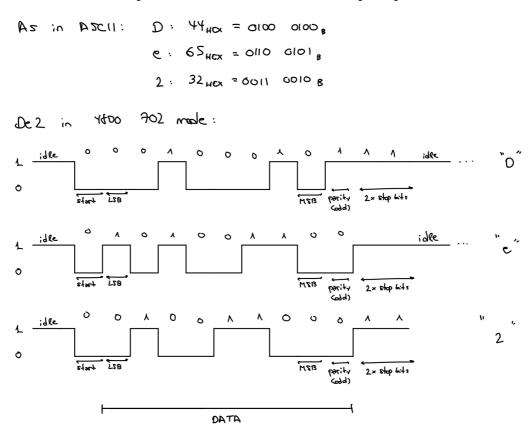1. (Hand-drawn) picture of UART signal when transmitting three character data De2 in 4800 7O2 mode (7 data bits, odd parity, 2 stop bits, 4800 Bd).



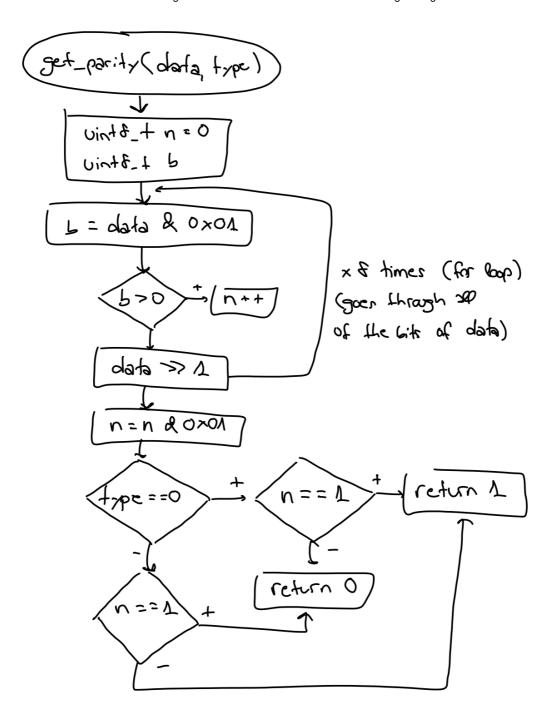2. Flowchart figure for function uint8_t get_parity(uint8_t data, uint8_t type) which calculates a parity bit of input 8-bit data according to parameter type. The image can be drawn on a computer or by hand. Use clear descriptions of the individual steps of the algorithms.



Temperature meter

Consider an application for temperature measurement and display. Use temperature sensor TC1046, LCD, one LED and a push button. After pressing the button, the temperature is measured, its value is displayed on the LCD and data is sent to the UART. When the temperature is too high, the LED will start blinking.

1. Scheme of temperature meter. The image can be drawn on a computer or by hand. Always name all components and their values.

